

EE 463

Electromechanical Energy Conversion

Term Project: DC Motor Driver

Project Report

Hakan Polat 2031243

Yunus Emre Balcioğlu 1936376

Mert Karaçelebi 2030930

1. Introduction

In this project we are asked to design a DC Motor driver. In this report the implementation procedure of a DC Motor driver will be explained in detail. In the first part of the report the problems will be listed. In the second part the solution possibilities, their advantages and disadvantages will be discussed. Then in the 4th part the simulation for the chosen solution will be performed. In the 5th part a theoretical lumped parameter thermal analysis will be made. According to the solution, simulations and thermal analysis the required equipment will be selected and explained more in detail. After the choice of equipment the implementation procedure will be explained and results of the design will be given. In the comment part any deviation from the theory and encountered problems will be discussed in detail and in the conclusion part a short summary of the Project will be made.

2. Project Definition

In this Project we are required to implement a controlled rectifier. Our input is 3 phase AC (i.e 400 V_{L-L} and frequency = 50 Hz) and our output is an adjustable DC output. The motor that will be driven is in Figure 1 and its specs are in Figure 2.



Figure 1: The image of the motor.

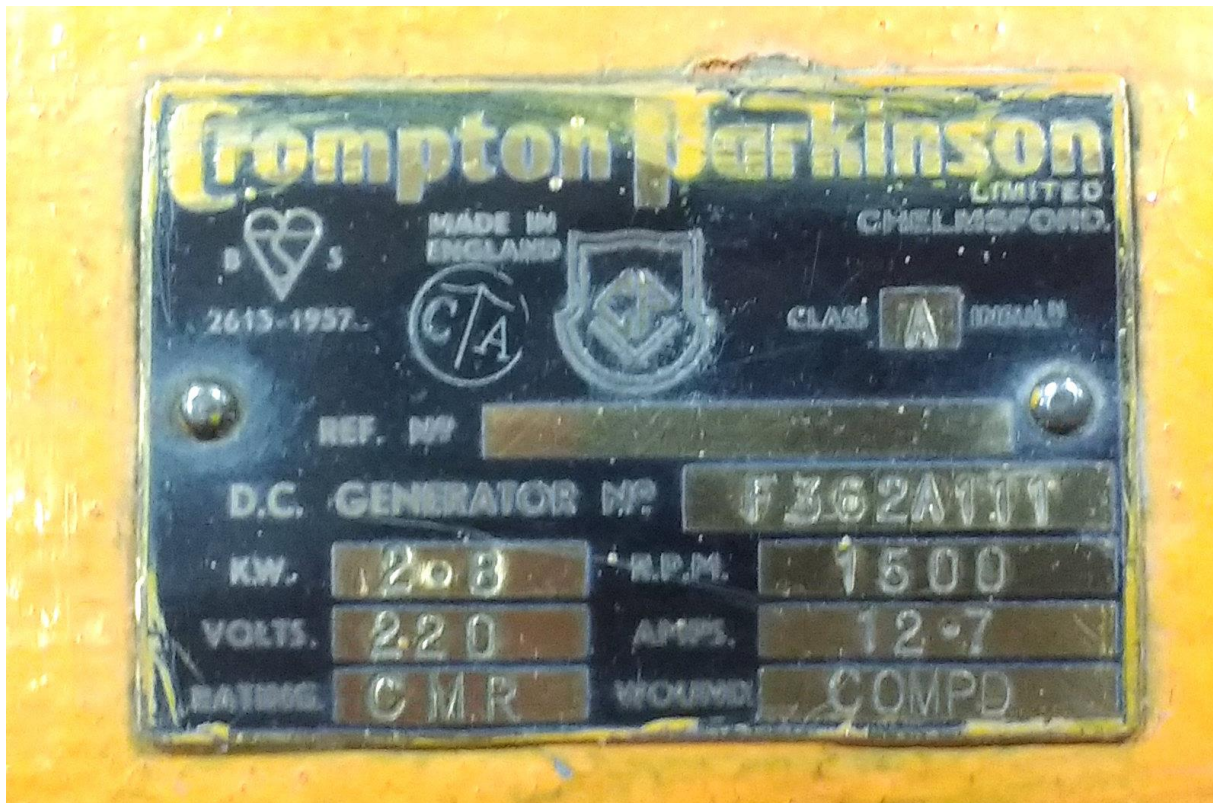


Figure 2: Rated values of the DC motor in Figure 1

- Armature Winding: 28Ω , 13.3 mH
- Series Winding: $65 \text{ m}\Omega$, 260 μH
- Shunt Winding: $8.26 \text{ k}\Omega$, 6.4 H
- Interpoles Winding: 0.8Ω , 5.8 mH

The connection impedance values are as above. In this Project we need to drive the motor under no load however as a bonus we also did under full load (2.8kW).

3. Solutions

During lecture hours we learned about diode, thyristor rectifiers and buck,boost and buck-boost converters. Since we are required to implement a controlled rectifier we have mainly 3 solutions.

- 3 Phase thyristor rectifier

The three phase thyristor rectifier requires 6 thyristors a DC-link capacitor, 6 gate driver circuits and a controller unit. It may be preferable over 1 phase thyristor rectifier since 3 phase rectifier output is more similar to a DC output. However implementing the gate driver circuit and the controller unit is a serious problem and challenge for our design. Also the firing angles should be synchronized with the phases.

- 3 Phase Diode rectifier+ Buck Converter

This solution requires a three phase diode rectifier, an IGBT, a diode, a DC link capacitor, gate driver circuit and a controller unit. This solution seems the easiest to implement since it requires only a single gate driver circuit and there is no other gate driver hence no synchronization problem like in the thyristor case.

- 3 Phase Diode + Boost Converter

This solution is similar to the solution with the buck converter however since what we are trying to control is the current input to the motor a boost converter is not preferable since boost converter increases the voltage however it reduces the current input.

Taking all solutions into consideration we decided to use a 3 phase diode rectifier + a buck converter.

- Gate Driver

In all of our solutions we require a gate driver circuit. Since micro controllers are prone to high voltage an isolation is necessary. We are planning to use an optocoupler (TLP250 or HCPL3120) for our gate driver circuit. Also we require a floating voltage source since we should have a junction voltage or a V_{gs} voltage above the threshold for PWM input. Hence an optocoupler satisfies our needs. As for the microcontroller we are planning to use Arduino. Although it is high in cost, for learning purposes it gives the flexibility of easy pwm generation and frequency and duty cycle adjustment. The circuit of the gate driver is in Figure 3.

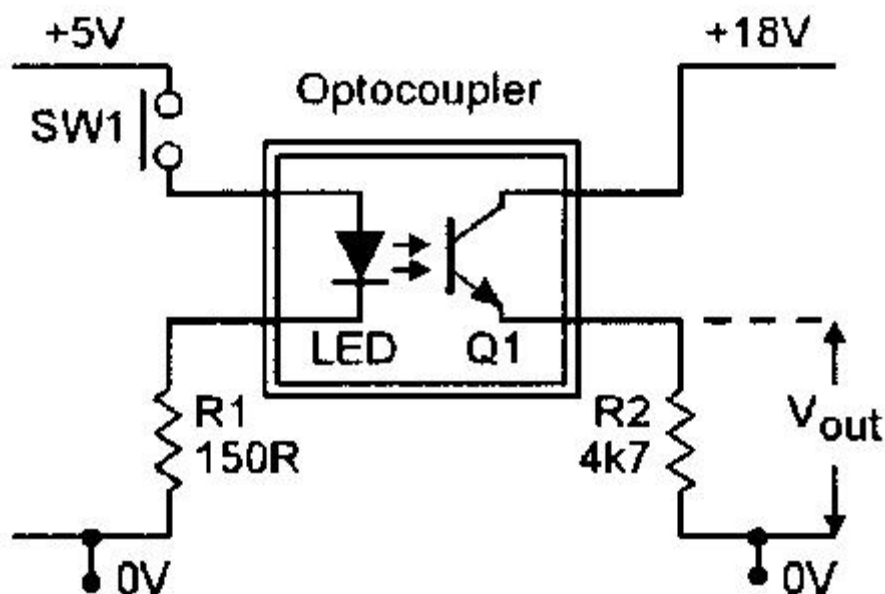


Figure 3: Gate driver using an optocoupler.

The PWM generated is connected to the left side of the optocoupler in Figure 3 (Led side).

External power is supplied from a DC power supply and the V_{out} is connected to the gate where the 0 V reference point is connected to the source(if MOSFET) or emitter (IGBT) or

anode(thyristor). The 150 ohm resistance in the controller side is for protection. Also a 100nF capacitor is connected between 18V and 0V for noise reduction. The external gate resistance is around 20 ohms.

- PWM Generation

The Arduino should generate a PWM signal for our solution. However Arduino is a simple PWM code does not work under high frequencies. Therefore a manipulation of the the Arduinos clock is necessary.

```
int POT = A0;
```

```
int PWM =13;
```

```
float Duty=0;
```

```
float D=0;
```

```
int divisor = 64;
```

```
void setup() {
```

```
    Serial.begin(9600);
```

```
    pinMode(PWM,OUTPUT);
```

```
    pinMode(POT,INPUT);
```

```
    TCCR2B = TCCR2B & B11111000 | B00000010; // set timer 2 divisor to 8 for PWM  
    frequency of 3921.16 Hz
```

```
}
```

```
void loop() {
```

```
    D=analogRead(POT);
```

```
    if (D<10){
```

```
        D=0;
```

```
        Serial.print("*****");
```

```
    }
```

```
    Duty=D/1024*255;
```

```
    analogWrite(PWM,Duty);
```

```
    delay(2000);
```

```
    Serial.print("The duty cycle is:");
```

```
Serial.println(D) ;
```

```
}
```

This arduino code takes voltage input from a potantiometer and gives an adjustable PWM with a frequency of 3900 Hz. The output pin is 13.

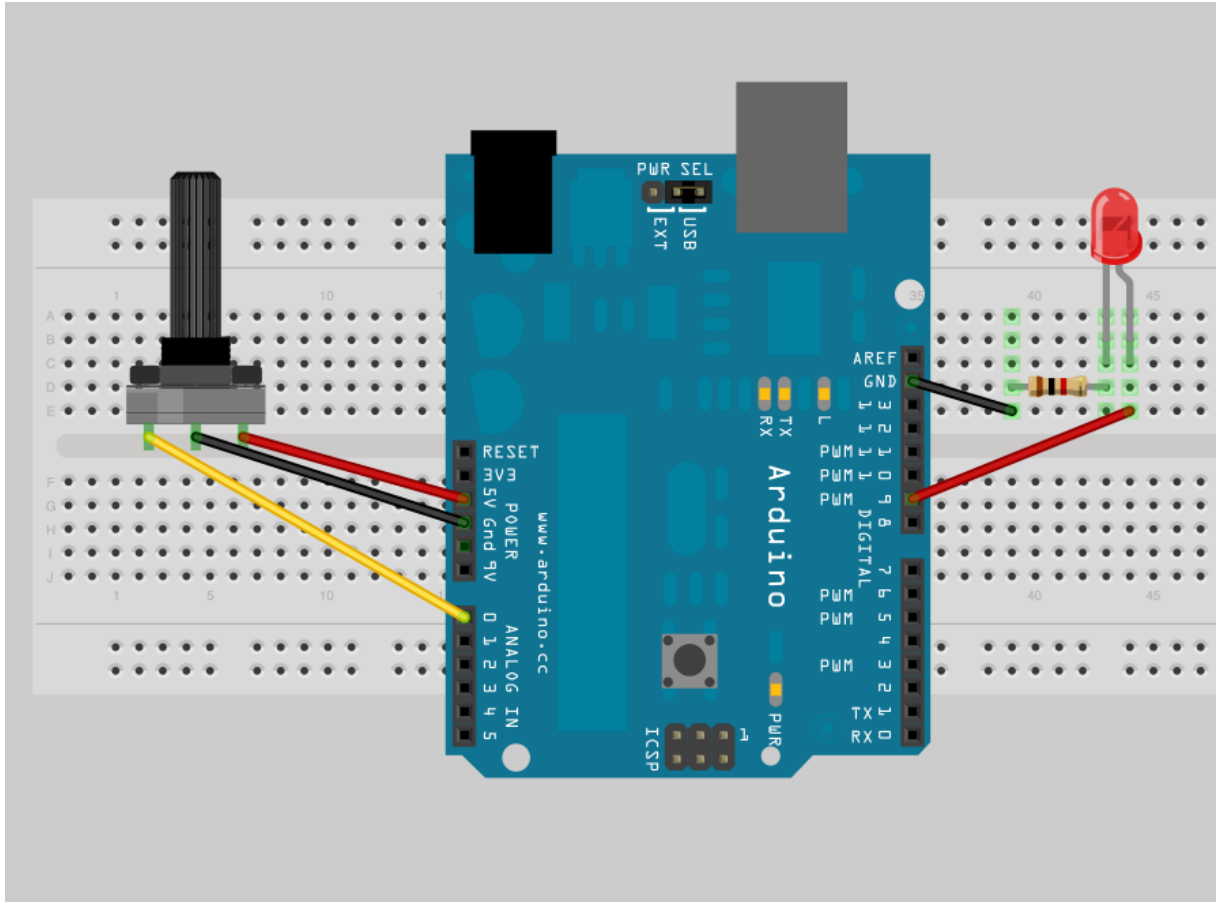


Figure 4: A sample Arduino connection

A sample Arduino connection is in Figure 4. The voltage input is taken from Analog 0 and PWM output is from PIN13. The led in Figure 4 is the led in gate driver circuit in Figure 3.

4. Simulation Results

In this part simulations will be made using MATLAB Simulink for several extreme cases like very low duty cycle and high duty cycle for equipment selection. During the simulations the gate driver circuit is replaced with a logic PWM signal.

The schematic for the simulation is in Figure 5.

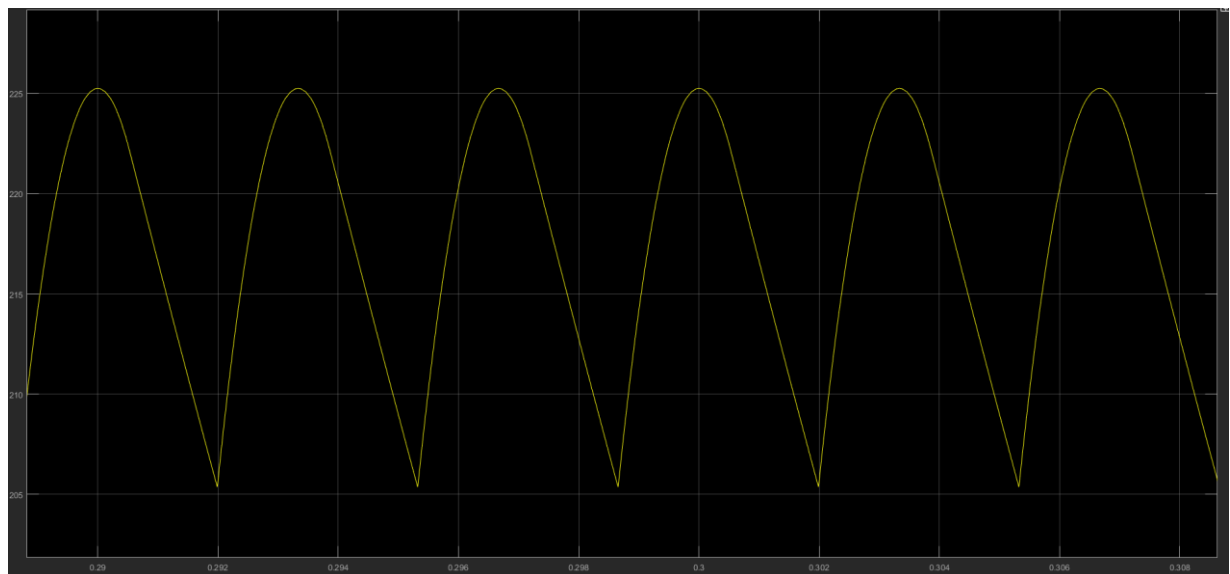


Figure 7: Motor Voltage

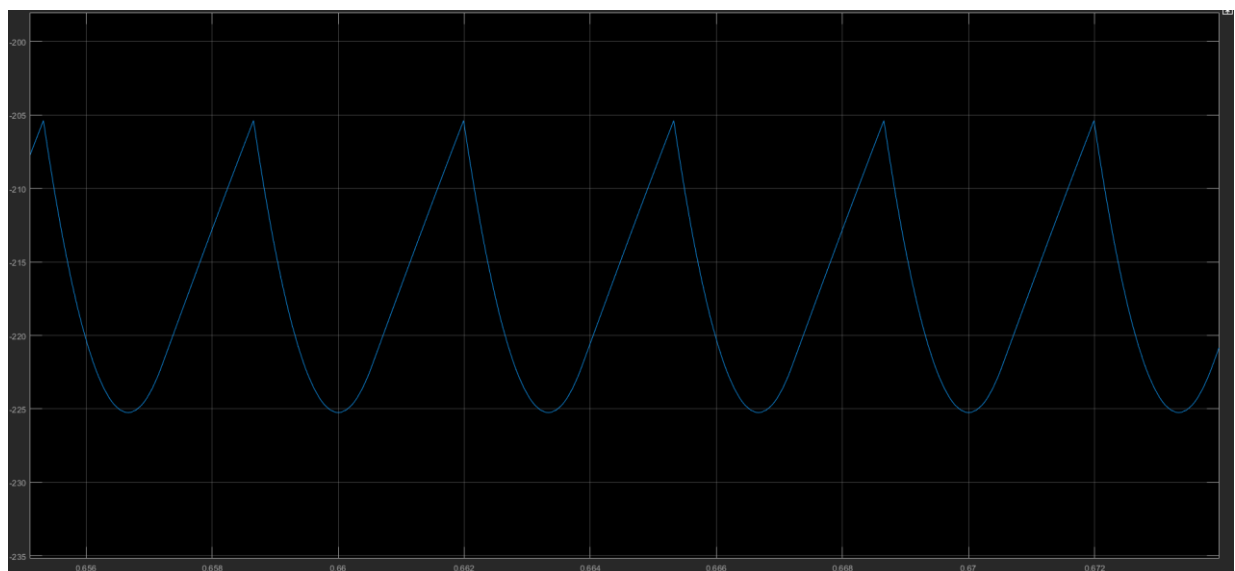


Figure 8: Diode Voltage

IGBT Voltage RMS	1 V
IGBT Current RMS	7A
Diode Voltage RMS	-220V
Diode Current RMS	0A
Capacitor Voltage RMS	220V
3 Phase Rectifier Voltage RMS	220V
3 Phase Rectifier line Current RMS	9A

- PWM Duty Cycle= 0.5

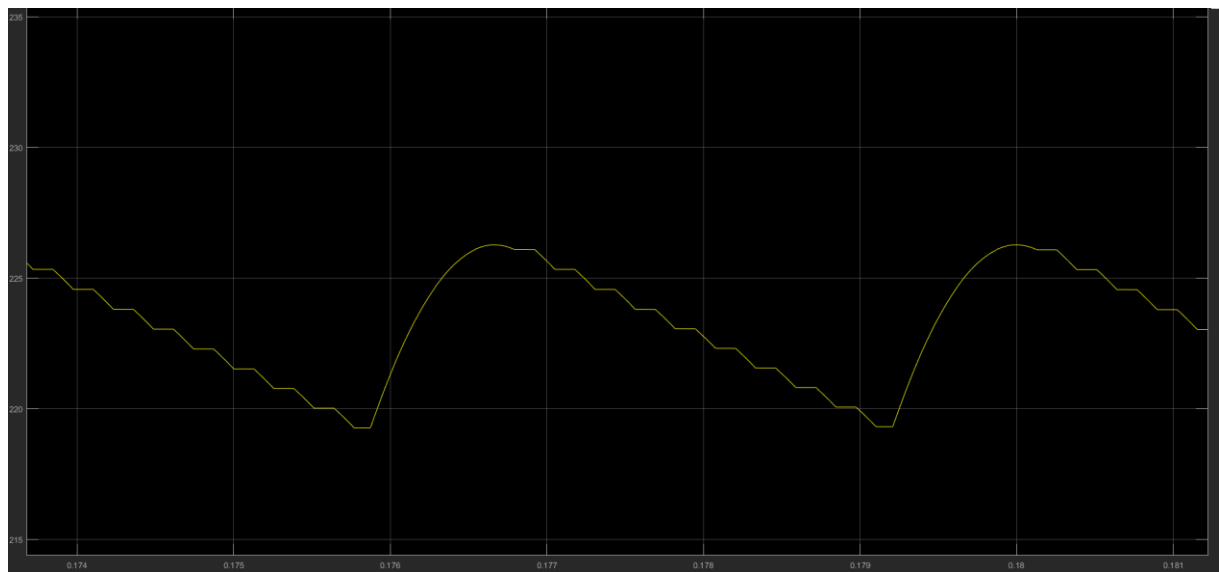


Figure 9: Voltage of the DC-link Capacitor i.e DC voltage input of the Buck Converter

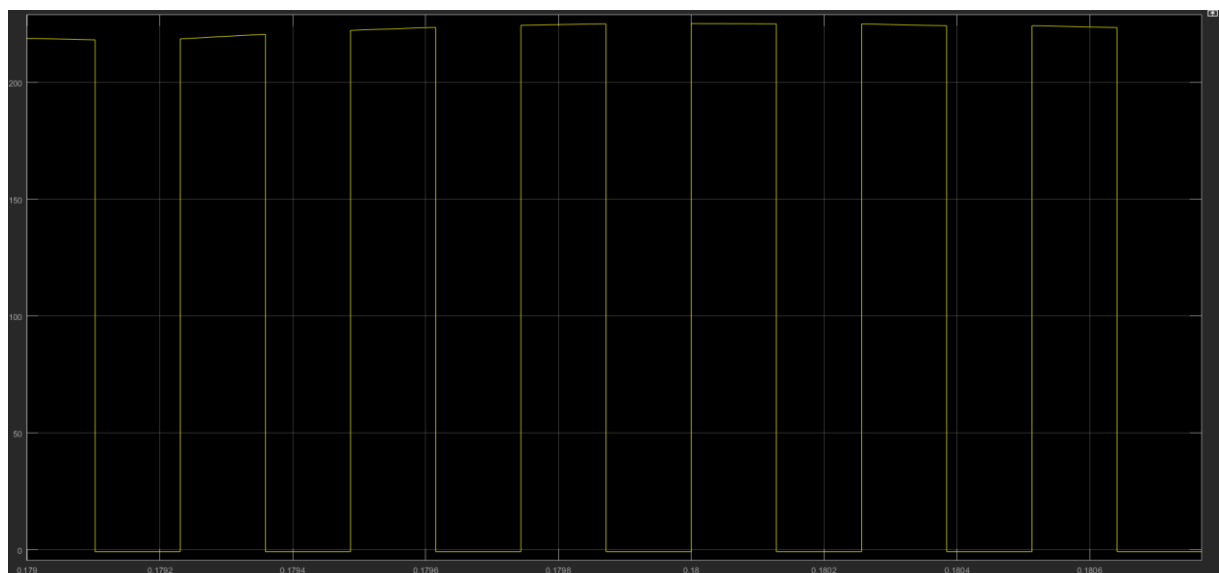


Figure 10: Motor Voltage

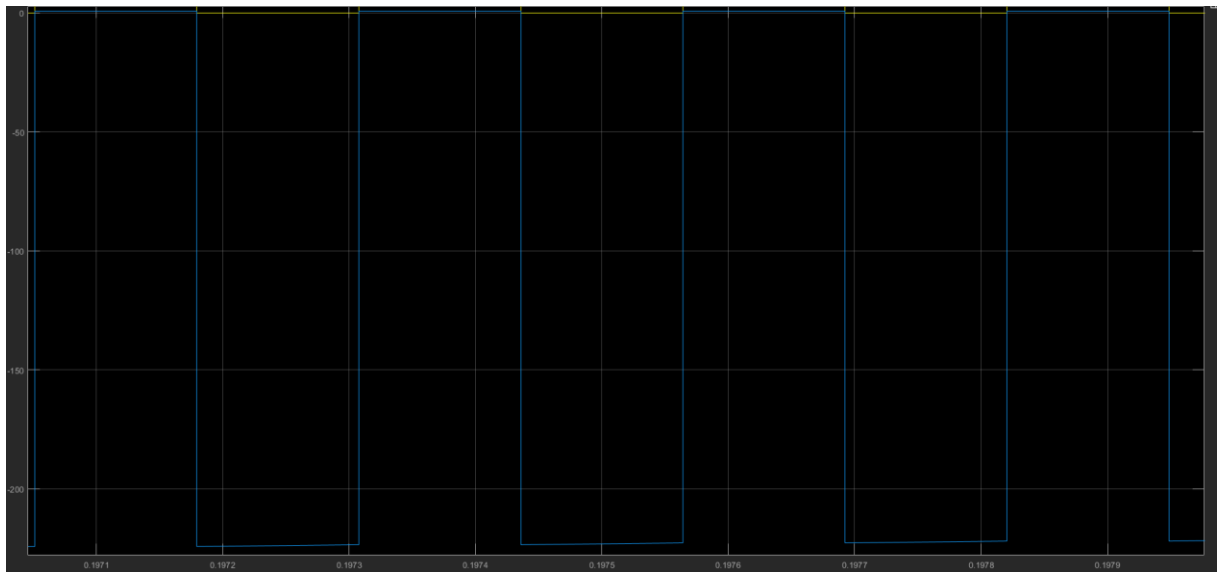


Figure 11: Diode Voltage

IGBT Voltage RMS	156 V
IGBT Current RMS	3 A
Diode Voltage RMS	-155 V
Diode Current RMS	2.26 A
Capacitor Voltage RMS	220 V
3 Phase Rectifier Voltage RMS	220 V
3 Phase Rectifier line Current RMS	3.8 A

- PWM Duty Cycle= 0

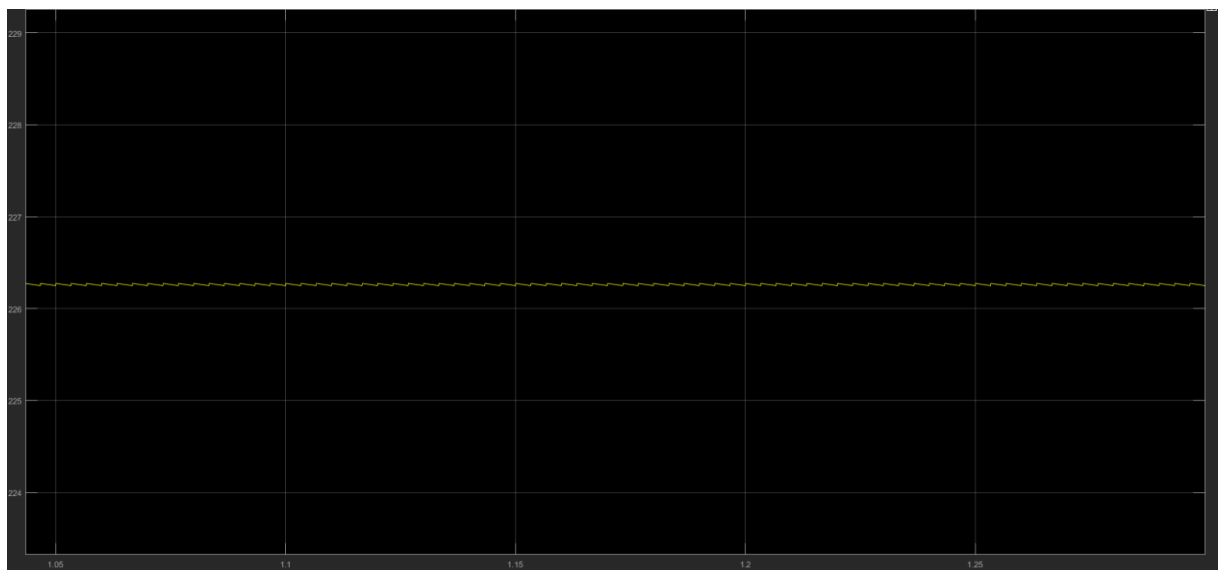


Figure 12: Voltage of the DC-link Capacitor i.e DC voltage input of the Buck Converter



Figure 13: Motor Voltage



Figure 14: IGBT Voltage

IGBT Voltage RMS	220 V
IGBT Current RMS	0 A
Diode Voltage RMS	0 V
Diode Current RMS	0 A
Capacitor Voltage RMS	220 V
3 Phase Rectifier Voltage RMS	220 V
3 Phase Rectifier line Current RMS	0 A

According to the simulations the equipment rated values should be above

IGBT Voltage RMS	220 V
IGBT Current RMS	7 A
Diode Voltage RMS	220 V

Diode Current RMS	7 A
Capacitor Voltage RMS	220 V
3 Phase Rectifier Voltage RMS	220 V
3 Phase Rectifier line Current RMS	9 A

For safety 1.5x of every rated value would keep us on the safe side.

5. Equipment Selection

After finding the rated value for equipment we can select our products. We investigated the several websites as Farnell or Texas Instruments. However those sites have shipping rates which is really expensive and delivery time is long. We selected our supplier as “Yıldırım Elektronik” which is located at center of the Ankara and prices are reasonable.

Our first fundamental component is 3 phase diode rectifier. For diode rectification we have two options. First option is construct the rectifier using 6 separate diodes. Second option is using a glass passivated bridge rectifier, that is a commercial product and more reliable, also cheaper than separate 6 diodes. That’s why we selected a three phase passivated bridge rectifier. At appendix A, one can find the related link to our product datasheet. In figure 15, one can find the picture of our rectifier.

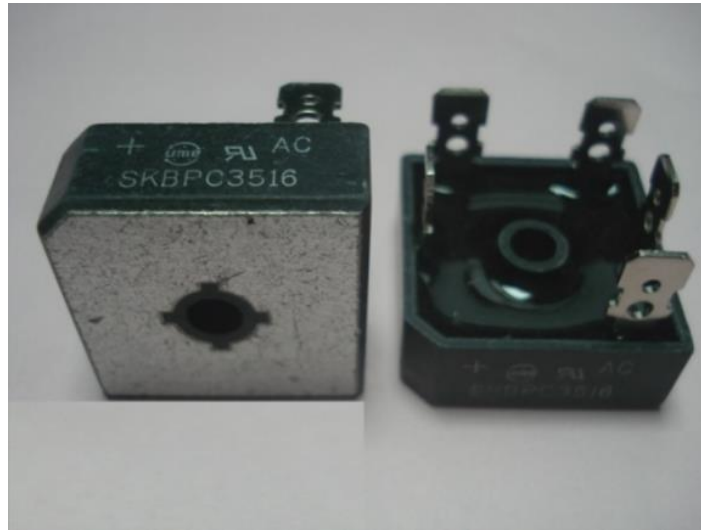


Figure 15: Picture of SKBPC3516

As one can see from the picture size of the rectifier is suitable and easy to make connections. In figure 16 one can find the rated values which we used in selection processes.

Parameter	Condition	Value	Unit
Repetitive Peak Reverse Voltage		1600	Volts
Average Rectified Output Current	With Heatsink at 55 Celsius/ 60 Hz sine	35	Amperes

	wave with RL load		
Junction Temperature		-40 to 150	Celsius
Thermal Resistance	Between Junction and Case with Heatsink	1.35	°C/W

Figure 16: Related Rated Values

Peak reverse voltage breakdown is high above for our project, but when we considered the current capability we selected SKPBC3516. Thermal resistance is used while our thermal analysis section, our product's thermal resistance smaller compared to other products.

Our Second equipment is DC Link capacitor. Compared to rectifier we have limited sources to obtain the capacitor for our rated values and we want to stay in safe side we selected our capacitor rating above the rated values. We selected "Kendeil "460 Volts, 680 μ F capacitor. As one can see from its rating it is designed for compensation in low voltage systems but it is suitable for our project too. In figure 17 one can find the picture of capacitor.



Figure 17: Picture of Kendeil Capacitor

ESR losses of capacitor is relatively low compared to series connected several capacitors. Buying several small capacitors compared to our product will be cheaper but for low loss and reliability we selected large capacitor.

Our next component is our switching transistor. First we used Mosfet transistors for switching purposes but we realized reliability issues occurred while operating at rush current regions of the motor in addition to this conduction, switching losses are higher than its peer IGBT. Compared to IGBT and Mosfet, IGBT has some disadvantages such as hard to drive its gate and expensive. However it is more reliable and less lossy than Mosfet. In figure 18, one can find the IXGH 32N90B2 IGBT transistor.



Figure 18: IGBT IXGH32N90B2

In figure 19 one can find the related information about the transistor.

$$\begin{aligned}
 V_{CES} &= 900 \text{ V} \\
 I_{C25} &= 64 \text{ A} \\
 V_{CE(sat)} &= 2.7 \text{ V} \\
 t_{fi \text{ typ}} &= 150 \text{ ns}
 \end{aligned}$$

$t_{d(on)}$	Inductive load, $T_J = 125^\circ\text{C}$ $I_C = I_{C110} \text{ A}, V_{GE} = 15 \text{ V}$ $V_{CE} = 720 \text{ V}, R_G = R_{off} = 5 \Omega$ Note 1	20	ns
t_{ri}		22	ns
E_{on}		0.5	mJ
		3.8	mJ
$t_{d(off)}$		360	ns
t_{fi}		330	ns
E_{off}		5.75	mJ
R_{thJC}			0.42 K/W
R_{thCS}	(TO-247)	0.25	K/W

Figure 19: Ratings of IGBT

First we investigate our ratings, it can be seen as an overdesign for this project but for safety reasons and to increase the lifetime of operation, this IGBT is suitable. Thermal resistances and switching losses are important for thermal analysis procedure.

Our next component is freewheeling diode. Since we are operating around 4 kHz switching frequency, we used Fast Recovery Epitaxial Diode (FRED) DSEI30-12A. At off stage of the switch all motor current will circulate through the freewheeling diode therefore

current/voltage rating of diode must be equal or higher than the motor ratings. In Figure 20, one can find the picture of diode.

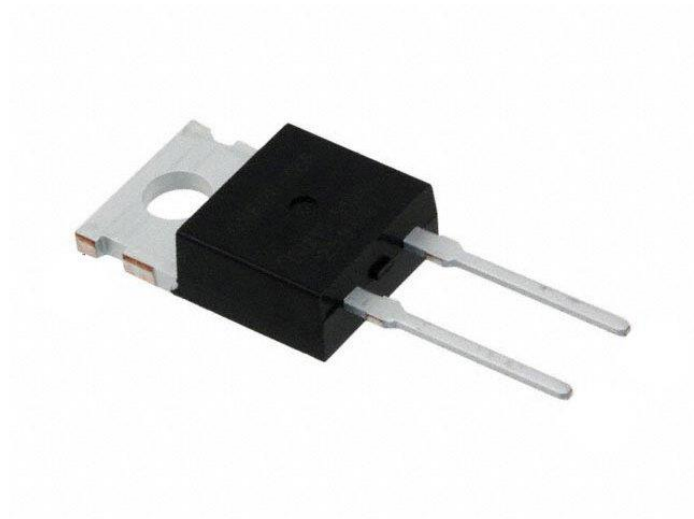


Figure 20: Picture of DSEI30-12A

In figure 21 one can find the related information about the diode.

$$\begin{aligned} I_{FAVM} &= 26\text{ A} \\ V_{RRM} &= 1200\text{ V} \\ t_{rr} &= 40\text{ ns} \end{aligned}$$

R_{thJC}			0.25	0.9	K/W
R_{thCK}					K/W
R_{thJA}				35	K/W
P_{tot}	$T_c = 25^{\circ}C$			138	W

Figure 21: Ratings of the diode

As one can see from the ratings current capability and voltage limit is high enough for operation. Also rise time is small enough compared to our switching frequency. Other parameters will be used during thermal analysis.

Our next component will be optocoupler HCPL 3120.Optocoupler is used for isolation between micro controller and gate driver circuit. In figure 22 one can find the picture of HCPL 3120 and in figure 23 one can find the ratings of the device.



Figure 22: Picture of HLCP 3120

LED	$V_{CC} - V_{EE}$ "POSITIVE GOING" (i.e., TURN-ON)	$V_{CC} - V_{EE}$ "NEGATIVE GOING" (i.e., TURN-OFF)	V_O
OFF	0 - 30 V	0 - 30 V	LOW
ON	0 - 11 V	0 - 9.5 V	LOW
ON	11 - 13.5 V	9.5 - 12 V	TRANSITION
ON	13.5 - 30 V	12 - 30 V	HIGH

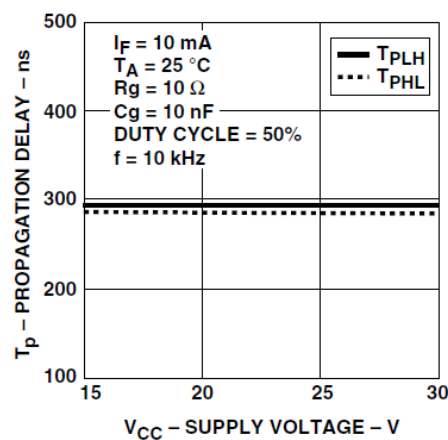


Figure 23: Related Information about HLCP 3120

As one can observe from the figure 23, propagation delay is relatively small compared to switching period. Also one can see the opening and closing regions of the optocoupler. We can get the High output when led is on and fed through the DC supply.

Our final equipment is a micro controller. For this project we used Arduino Mega but any microcontroller with fast clock cycle can be used for this purpose. Because only work of Arduino is, adapting the PWM signal according to measured voltage from the potentiometer.

6. Thermal Analysis

Thermal analysis can be done in various ways. Finite element analysis, computational fluid analysis, experimental or theoretical analysis can be done. First two method is complex to do and we can't model the ambient and location of components accurately. Therefore, we used theoretical approach for each element separately. Power input is modelled as current source, we have already known the thermal resistances of equipment and ambient temperature is selected as 30°C for machinery laboratory. After this analysis we can calculate the required thermal resistance of the heat sink when components are operating at 105 °C. In figure 24 one can find the sample thermal circuit.

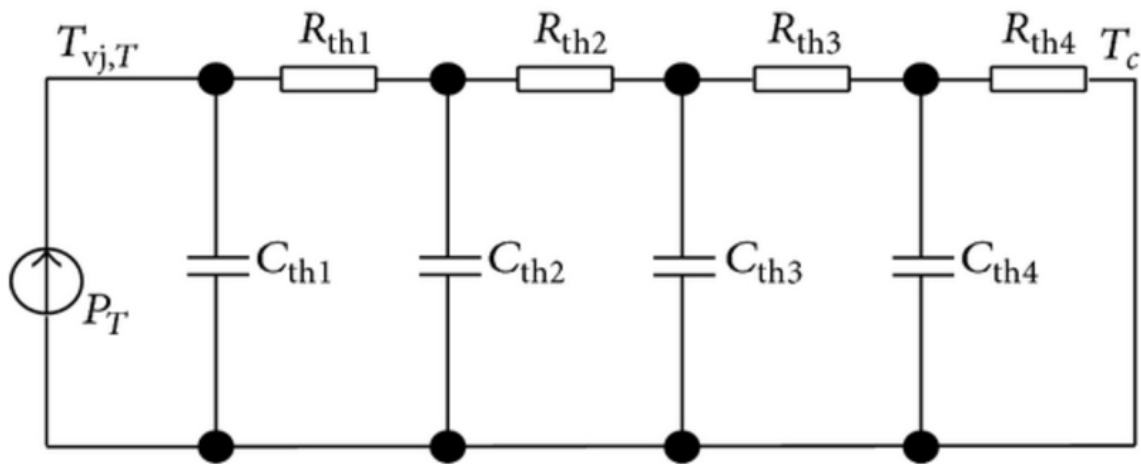


Figure 24: Sample Thermal Circuit

For simplicity we assume operating at steady state at 105 °C, so thermal capacitances can be neglected. First we have to calculate conduction and switching losses for freewheeling diode and IGBT. We can use formula 1 for conduction losses and formula 2 for switching losses.

$$P_c = V_{th} * I_{rms} * D$$

Formula 1: Conduction Losses

For voltage drop between terminals V_{th} can be found from datasheets, I_{rms} is equal to rating DC current flows through the motor and duty cycle is selected %50.

$$P_s = (E_{on} + E_{off}) * f_s$$

Formula 2: Switching Losses

All related datas can be found in datasheets. Calculated power losses can be found at table below. All power losses are calculated for full load case.

Component	Total Power Loss (W)
3-Phase Diode Rectifier	86.4
IGBT	55.39
Fast Recovery Diode	68

Using the thermal resistances given in equipment selection section we can use the following formula to calculate required heat sink size.

$$\Delta T = P * R_{th}$$

Using the case temperature for 105 °C and ambient 30 °C, resultant thermal resistances can be found as:

Component	Thermal Resistance Required (°C/Watt)
3-Phase Diode Rectifier	48
IGBT	65
Fast Recovery Diode	57

1 inch of 1 ounce aluminium heat sink is appropriate for all components. Since all design is contained in a closed box we used fans to circulate air inside the box.

7. Results



Figure 25: Optocoupler output voltage at 3.9kHz and 100% Duty Cycle

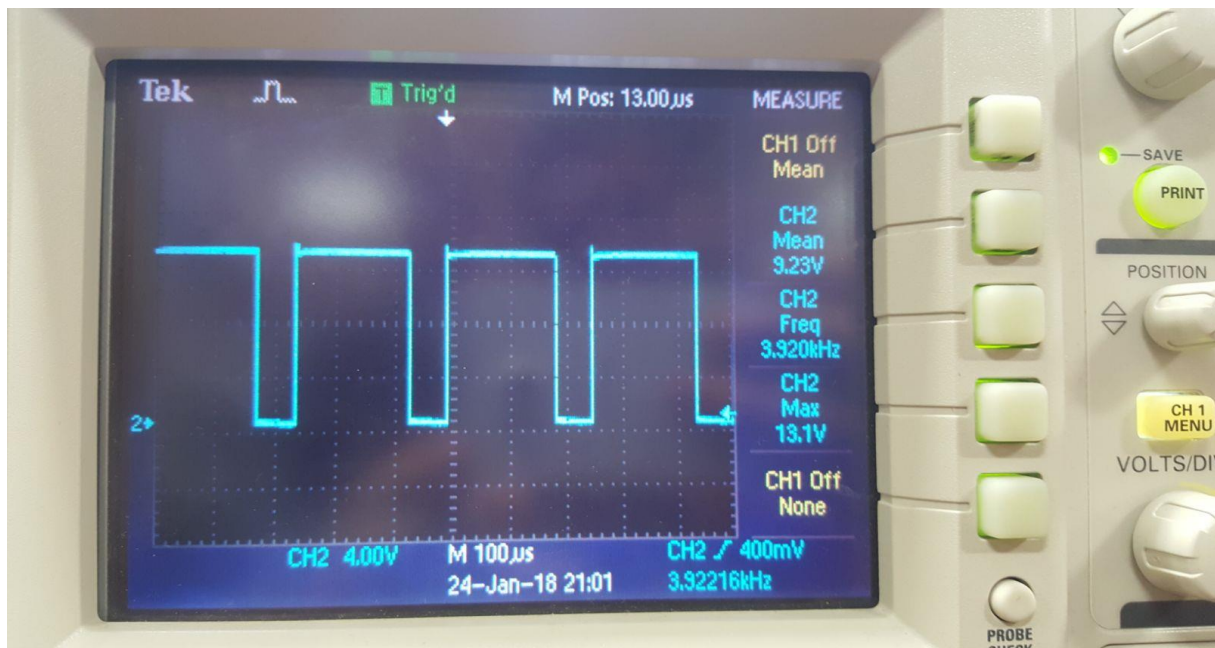


Figure 26: Optocoupler output voltage at 3.9kHz and 75% Duty Cycle

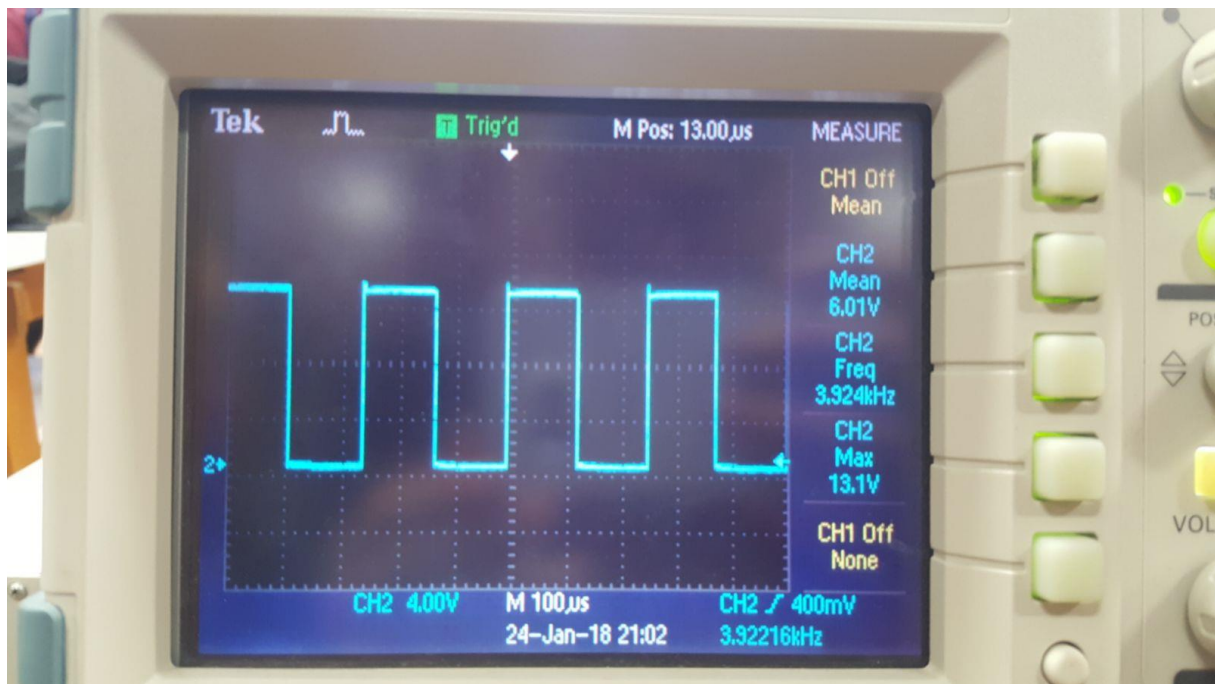


Figure 27: Optocoupler output voltage at 3.9kHz and 50% Duty Cycle

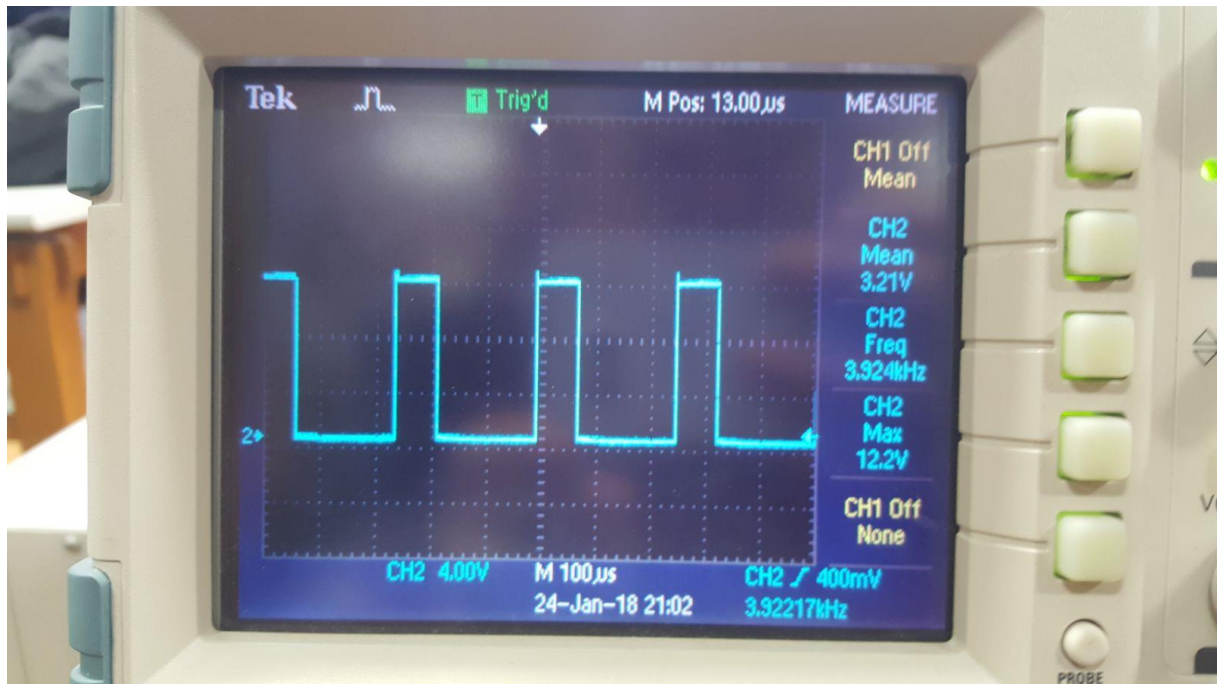


Figure 28: Optocoupler output voltage at 3.9kHz and 25% Duty Cycle

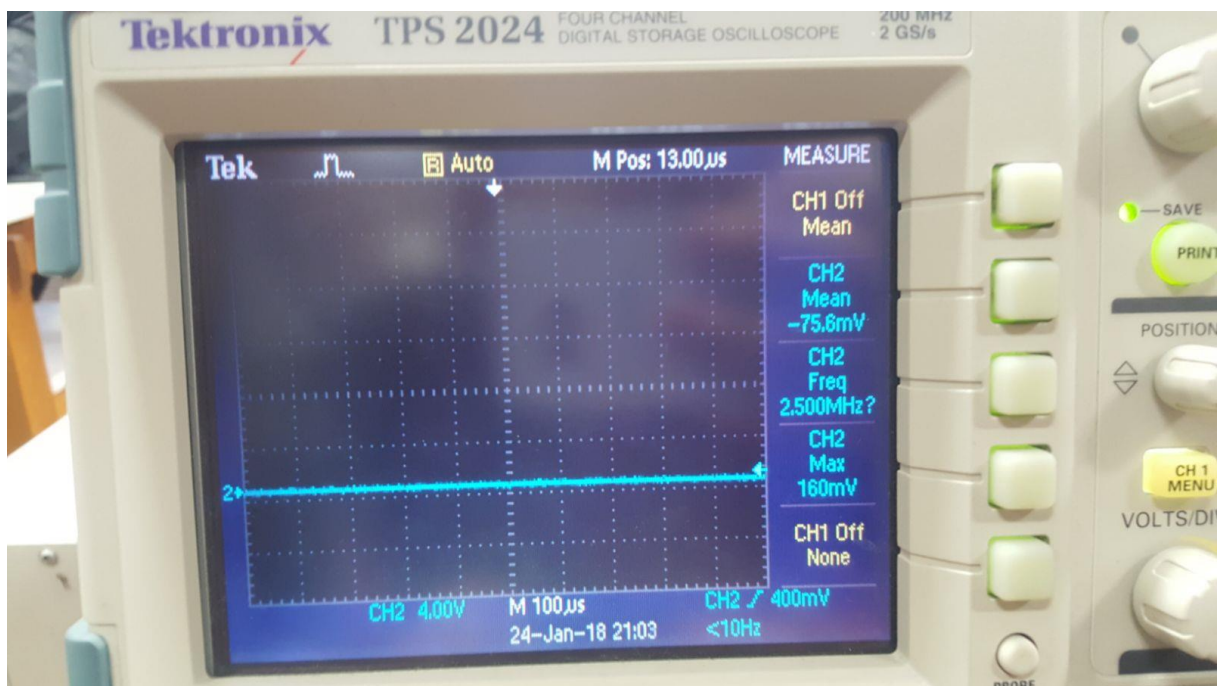


Figure 29: Optocoupler output voltage at 3.9kHz and 0% Duty Cycle

We got optocoupler outputs as shown above. Output waveforms are sufficient for our aim which is to control output voltage of buck converter. Frequency of duty cycles are 3.924 kHz.

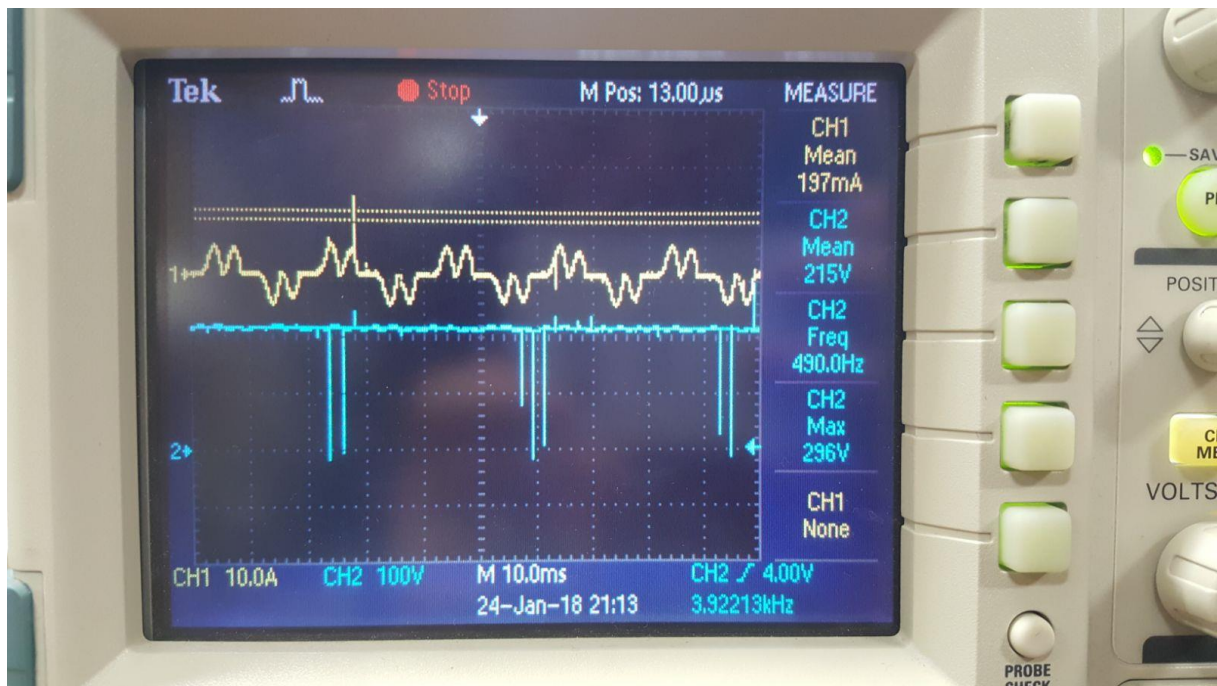


Figure 30: DC motor armature terminal voltage and line current wave forms at 100% Duty Cycle



Figure 31: Line current THD values at 100% Duty Cycle

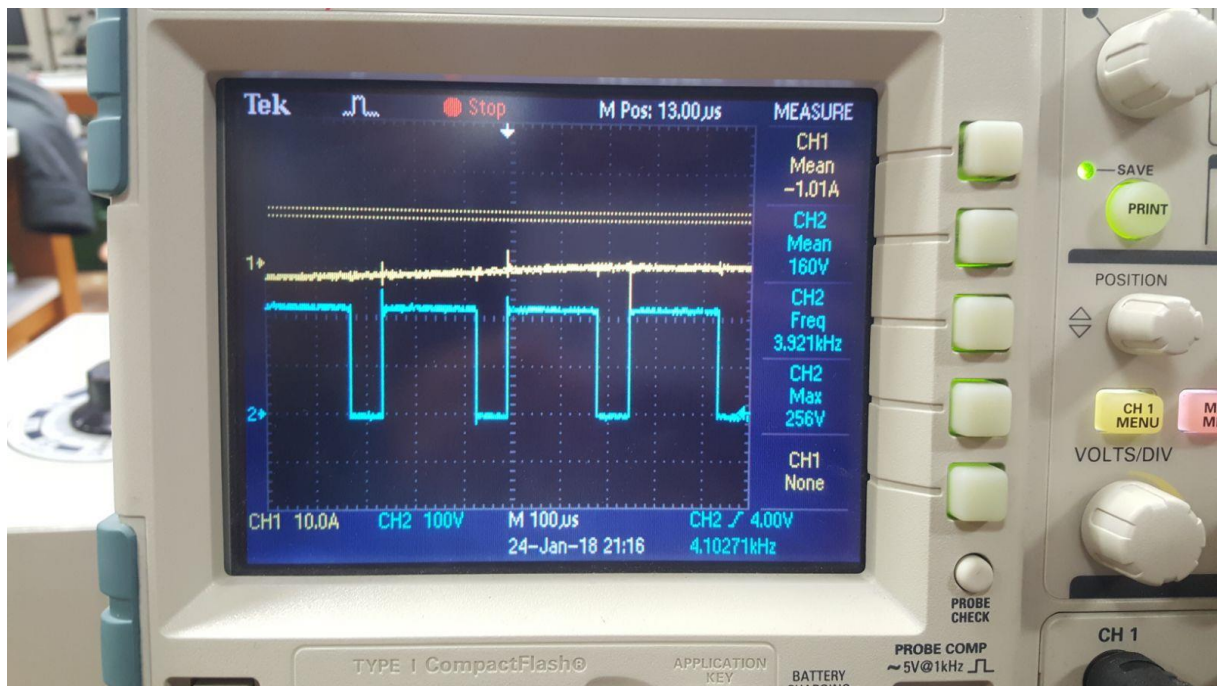


Figure 32: DC motor armature terminal voltage wave form at 75% Duty Cycle

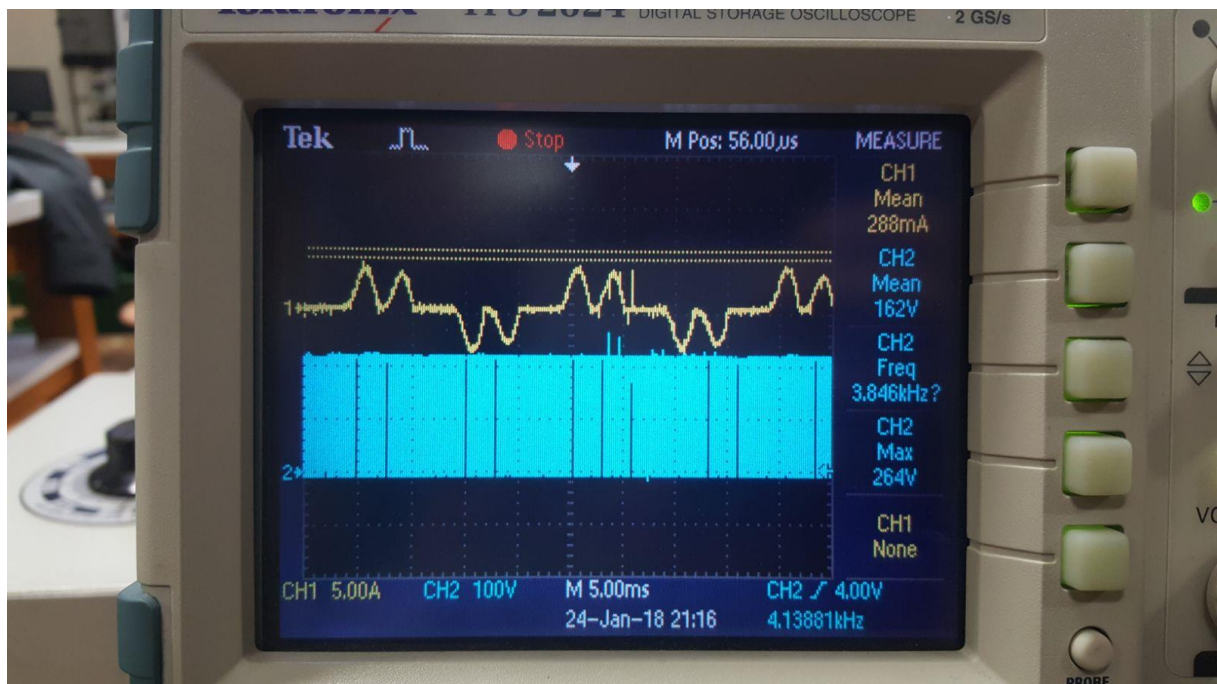


Figure 33: Line current wave form at 75% Duty Cycle



Figure 34: Line current THD values at 75% Duty Cycle

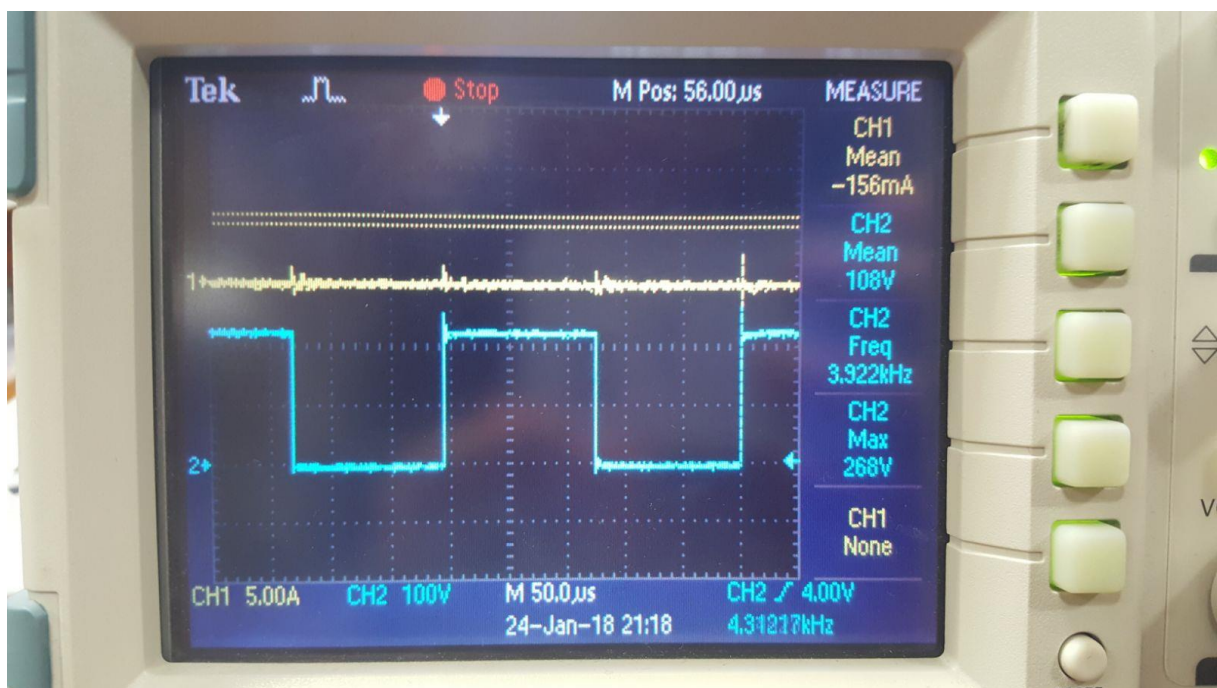


Figure 35: DC motor armature terminal voltage wave form at 50% Duty Cycle

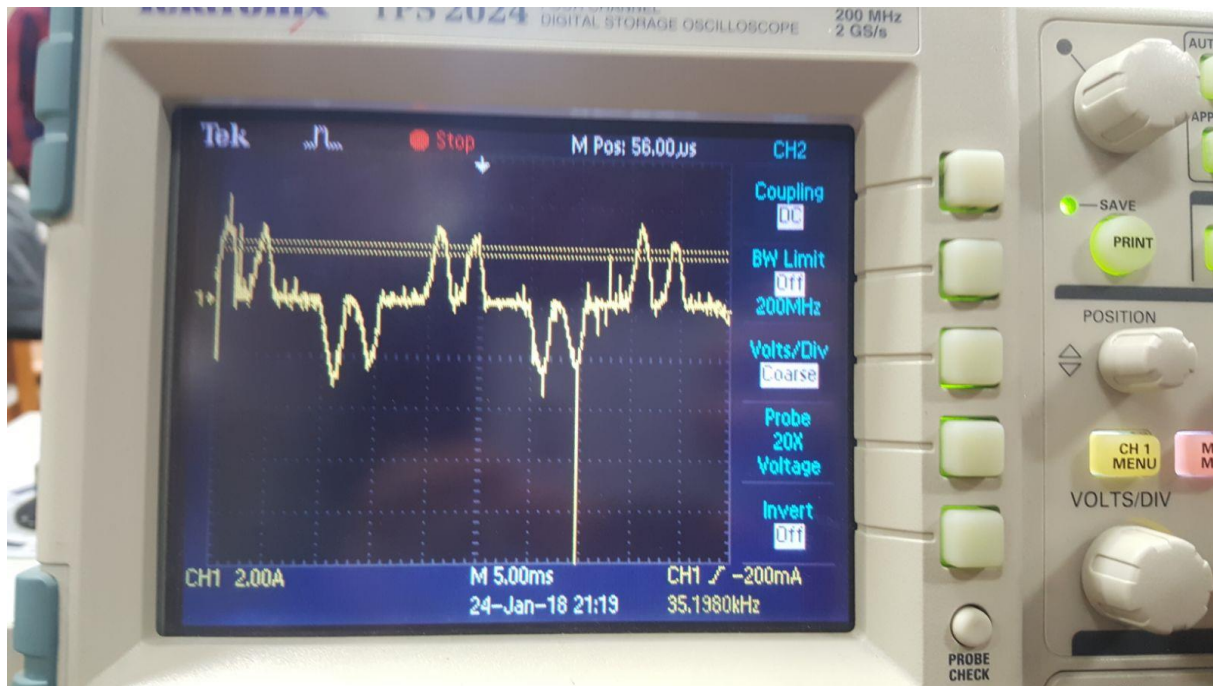


Figure 36: Line current wave form at 50% Duty Cycle



Figure 37: Line current THD values at 50% Duty Cycle

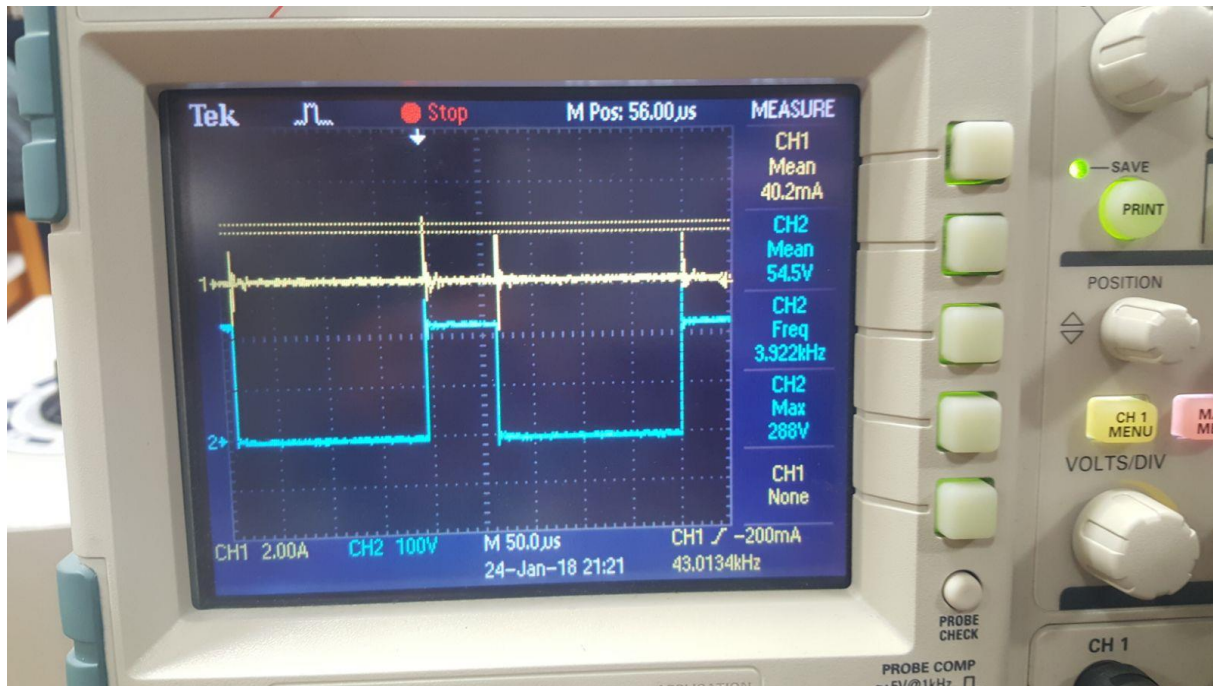


Figure 38: DC motor armature terminal voltage wave form at 25% Duty Cycle

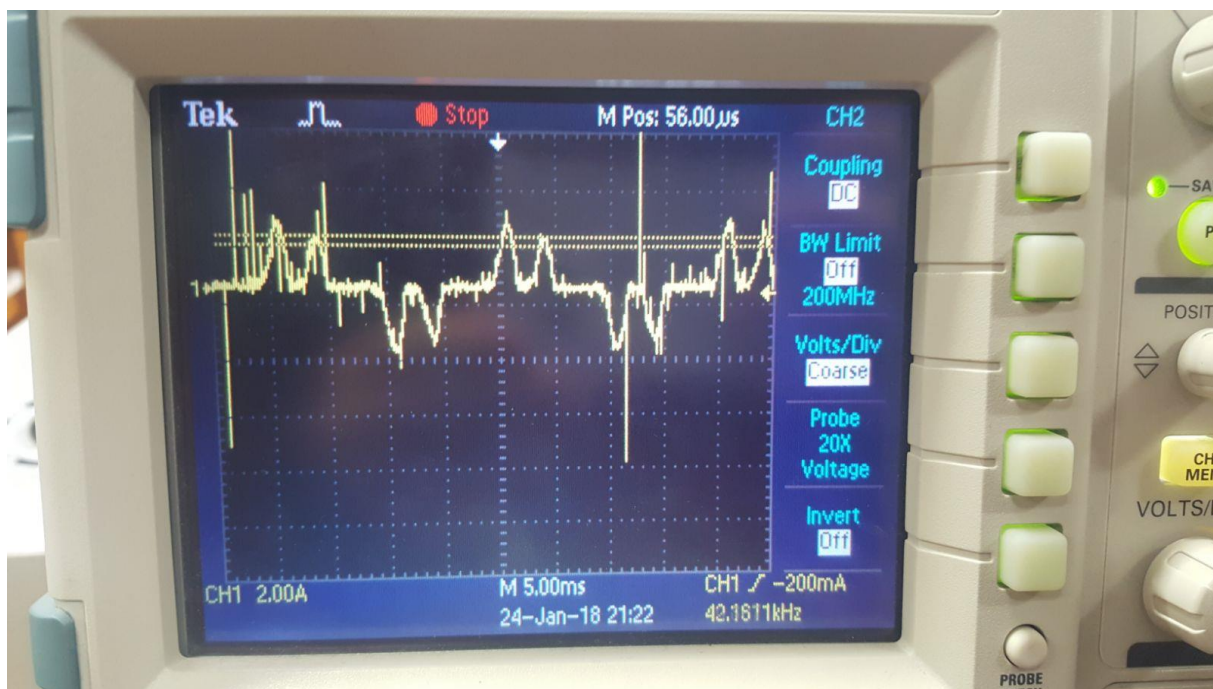


Figure 39: Line current wave form at 25% Duty Cycle



Figure 40: Line current THD values at 25% Duty Cycle

Duty Cycle	Mean of motor voltage(V)	Line current(A _{RMS})	Line current THD-F (%)	Motor speed(rpm)
100%	215	2.49	68	1500
75%	160	2.27	15.3	1336
50%	108	1.29	87.2	1204
25%	54.5	0.9	95.6	990

For %75 duty cycle line current THD value is 15.3%. Most probably, we got wrong result. If we consider the trend, when duty cycle is decreased THD increases.

When measuring these datas, field terminal of DC motor is powered by armature terminal of DC motor. Line current is measured 8 A due to this reason, and did not changed significantly. We measured armature current by using analog amperemeter.

When duty cycle is decreases, armature voltage decreased as expected, and result of this motor speed is decreased. Motor output power is Torque*MotorSpeed.

$$P_{IN} - P_{LOSS} = P_{OUT}$$

We did our measurements at no load, and output torque was constant, so when motor speed is decreased, P_{out} also decreased. If we assume P_{LOSS} is constant, and V_{IN} is constant. This situation explains why line current decrease when motor speed and duty cycle decreased.

Armature voltage waveforms and optocoupler output voltage waveforms make an agreement. This shows us our switching quality.

Mean of DC link capacitor voltage is 220 V.



Figure 41: Thermal photograph of 3-phase bridge rectifier



Figure 42: Thermal photograph of IGBT

These thermal photographs are taken under DC motor full load working period. 3-phase bridge rectifier is at 117.9 degree, and IGBT is at 74.7 degree. During DC motor no load working period highest temperature of components was 43 degree. When full load working period motor draws 12 A. It results this temperature increase.

8. Conclusion

In this project we designed an AC-DC converter-motor driver with a variable speed control. First we had done simulations on Mat-Lab Simulink environment. Up to this point we used our theoretical knowledge. After selecting the components we started to implement our design. In this manner we had several problems during montage of the equipment; we can even damage the components. Furthermore, we observed power electronic circuits must be handled carefully to eliminate unwanted situations such as voltage peaks which can terminate devices, high current values that cause unwanted heating problems. After achieved the successful operation we observed output voltages on motor side as expected in simulations. We observed the effect of applying pwm waveform to DC motor to control its speed by armature current control method. We observed sudden changes in duty cycle causes high voltage peaks at switching points. This type of real time problems can be harmful for the operation time of circuit. In overall this project is really helpful for us to understand real life problems in power electronic circuits and understand the importance of measurements. These measurements guide us to find the problems. Finally, in this project we had a chance to apply our practical skills with our theoretical knowledge.